

Simple transistor-based interface to connect an electronic speedo sender pulse stream to a Terratrip 202+ or 303+

Total parts cost: AUD 1.00 or less

Solder 10k resistor to base lead of BC548, then solder three different coloured insulated wires to the resistor and the two other transistor leads. Record which colour is connected to which lead. Then cover interface assembly with heat-shrink tubing, and connect the three wires to the vehicle speedo pulse cable and to the Terratrip 12 pin plug.

Caution:

Pinout for BC548 *et al* varies depending on package - this front view assumes the package is TO92 type 72 (std) which is C-B-E when looking at front face as shown. Check your BC548 with a transistor-checking multimeter.

